

Wroclaw University of Science and Technology

GENERAL PHYSICS LABORATORY REPORT

Theme of class: DETERMINATION OF SOLID
STATE DENSITY

Students:

1. Ivan Melnyk 275510
2. Egemen Goncu 276829

Date of class: 2023-03-14

Submission Date: 2023-03-07

Lab assistant: dr inz. Janusz Bozym

Contents

1	Introduction	2
1.1	Theory	2
2	Experiment	3
2.1	Determination of capacitance C of the capacitor component(RC circuit) . . .	3
2.2	Determination of the inductance L of the inductor component (RL circuit) .	4
2.3	Verification of the Ohm's Law for the alternation current (RLC circuit) . . .	5
3	Conclusion	7

1 Introduction

1.1 Theory

2 Experiment

2.1 Determination of capacitance C of the capacitor component (RC circuit)

dfsdlkfj

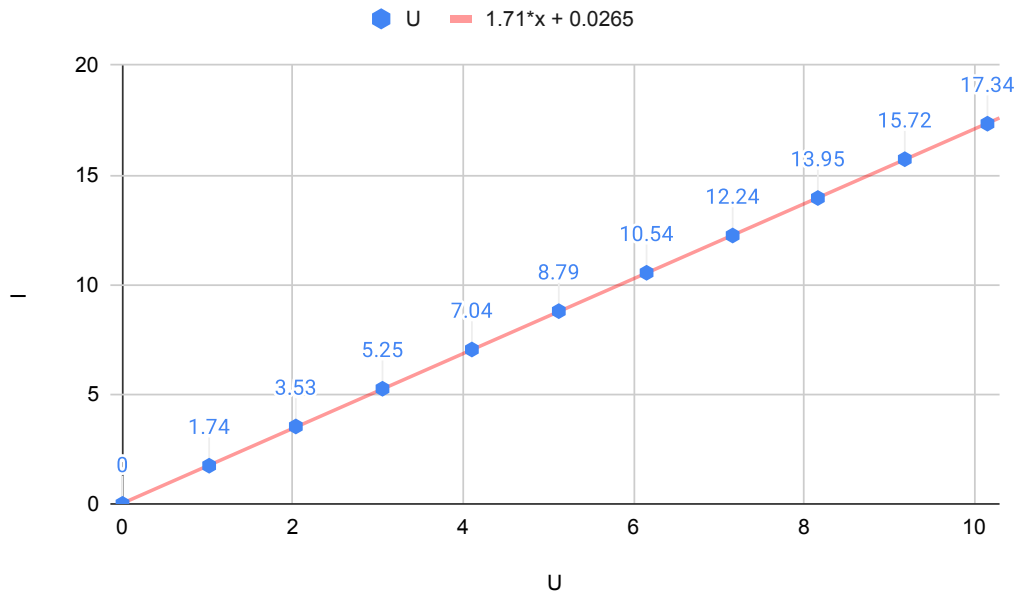


Figure 1: RC circuit measurements

V	UV	I mA
0	0	0
100	1.017	1.74
200	2.034	3.53
300	3.051	5.25
400	4.1	7.04
500	5.12	8.79
600	6.15	10.54
700	7.16	12.24
800	8.16	13.95
900	9.18	15.72
1000	10.15	17.34

Table 1: RC circuit. $f = 300 \text{ Hz}$
 $R = 220 \, \Omega$ $Z_c = 1.71 \text{ k}\Omega$

Calculations

$$C = \frac{1}{2\pi f \sqrt{(Z_c^2 - R^2)}} = \frac{1}{2\pi 300 \sqrt{(1.71^2 - 220^2)}} = 0.000000411562347 \quad (1)$$

2.2 Determination of the inductance L of the inductor component (RL circuit)

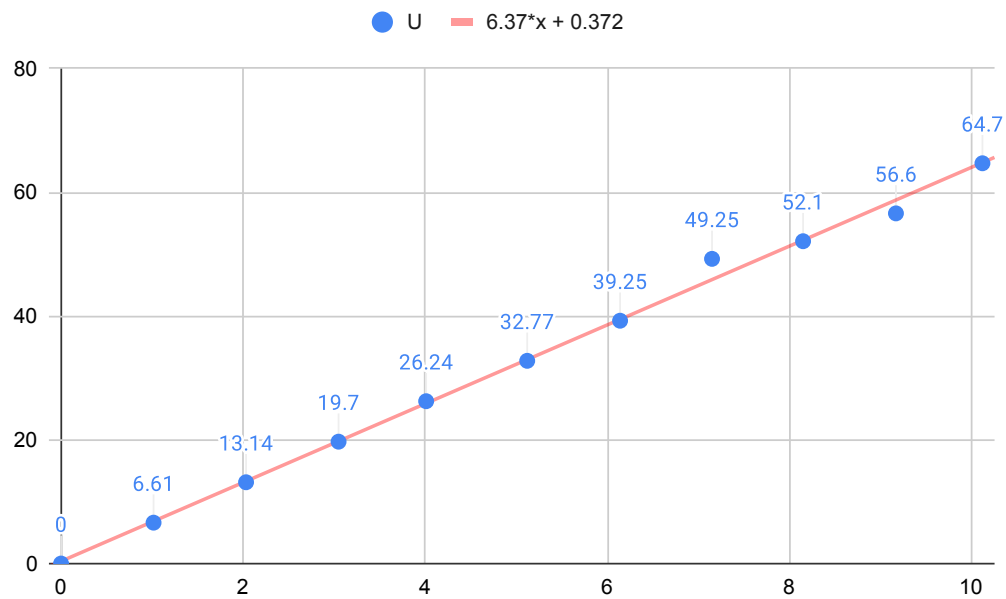


Figure 2: RC circuit measurements

Vrms	UV	ImA
0	0	0
100	6.61	1.016
200	13.14	2.032
300	19.7	3.048
400	26.24	4.01
500	32.77	5.12
600	39.25	6.14
700	49.25	7.15
800	52.1	8.15
900	56.6	9.17
1000	64.7	10.12

Table 2: RL circuit. $f = 300 \text{ Hz}$
 $R = 220 \Omega$ $R_l = 0.6 \Omega$ $Z_c = 6.37 \text{ k}\Omega$

Calculations

$$L = \frac{\sqrt{Z_L^2 - (R + R_L)^2}}{2\pi f} = \frac{\sqrt{6370^2 - (220 + 0.6)^2}}{2\pi 300} = 1.333838664 \quad (2)$$

2.3 Verification of the Ohm's Law for the alternation current (RLC circuit)

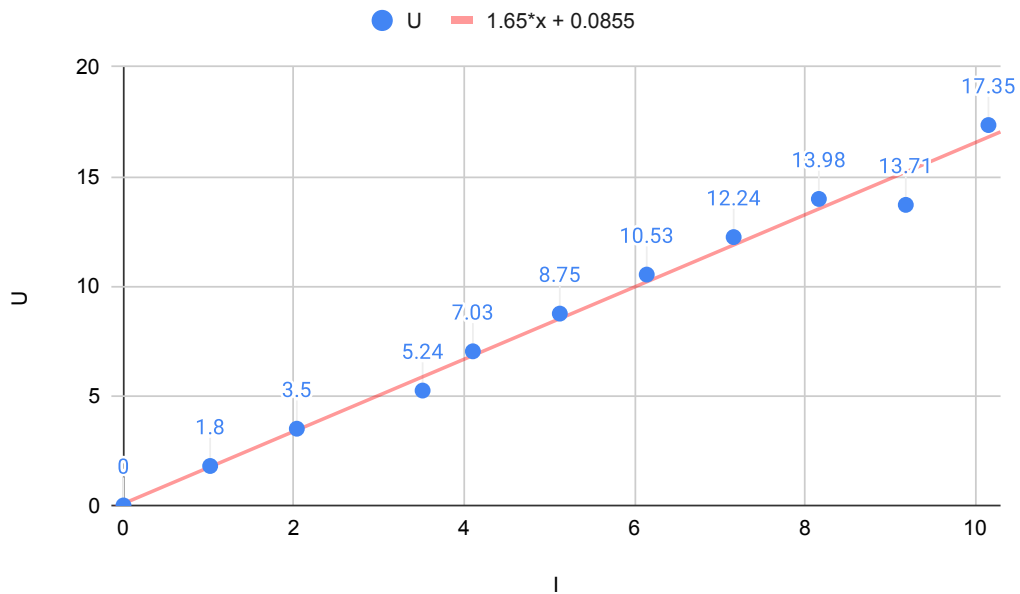


Figure 3: RC circuit measurements

V _{rsm}	U	I
0	0	0
100	1.8	1.017
200	3.5	2.034
300	5.24	3.51
400	7.03	4.1
500	8.75	5.12
600	10.53	6.14
700	12.24	7.16
800	13.98	8.16
900	13.71	9.18
1000	17.35	10.15

Table 3: RCL circuit. $f = 300 \text{ Hz}$
 $R = 220 \Omega$ $R_l = 0.6 \Omega$ $Z_{cl} = 1.65 \text{ k}\Omega$

Calculations

$$\begin{aligned}
 Z_2 &= \sqrt{(R + R_L)^2 + \left((2\pi fL) - \left(\frac{1}{2\pi fC} \right) \right)^2} = \\
 &\sqrt{(220 + 0.6)^2 + \left((2\pi 300 \times 1.333838664) - \left(\frac{1}{2\pi 300 \times 0.000000411562347} \right) \right)^2} = \\
 &1244.89743 \quad (3)
 \end{aligned}$$

Formulas used in the calculations

$$C = \frac{1}{2\pi f \sqrt{(Z_c^2 - R^2)}} \quad (4)$$

$$L = \frac{\sqrt{Z_L^2 - (R + R_L)^2}}{2\pi f} \quad (5)$$

$$Z_2 = \sqrt{(R + R_L)^2 + \left((2\pi fL) - \left(\frac{1}{2\pi fC} \right) \right)^2} \quad (6)$$

3 Conclusion